

# ECT 213 – Lecture 3

Chapter 3

Logic Gates  
Truth Tables

Chapter 5

Boolean Equations

---

---

---

---

---

---

---

---

## Logic Gates:

Building blocks for basic digital electronic circuits.

Output will be High (1) or Low(0)

## Truth Table:

Graphically displays output in table form.

---

---

---

---

---

---

---



---

## 2-Input AND Gate

Truth Table

Input		Output
A	B	Y
0	0	
0	1	
1	0	
1	1	

Boolean Equation:

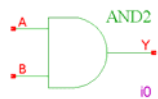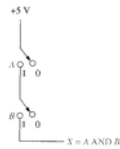

---

---

---

---

---

---

---

---

### Example – 2 Input And Gate Timing Diagram

	t <sub>0</sub>	t <sub>1</sub>	t <sub>2</sub>	t <sub>3</sub>	t <sub>4</sub>	t <sub>5</sub>	t <sub>6</sub>	t <sub>7</sub>	t <sub>8</sub>	t <sub>9</sub>
A	0	0	1	1	0	0	1	1	0	0
B	0	0	0	1	1	1	1	0	0	1
Y										

---

---

---

---

---

---

---

---

### 3-Input AND

Input			Output
A	B	C	Y



Boolean Equation

---

---

---

---

---

---

---

---

### Example – Burglar Alarm

Create a circuit that will sound an alarm when the alarm is armed and the door is opened.

Inputs

Output

---

---

---

---

---

---


---

---

## Example Circuit

Given the following Boolean equation,  
Wire it using the 74LS08 IC

$$X = A \cdot B \cdot C$$

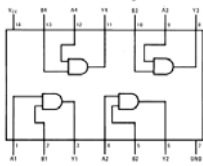


---

---

---

---

---

---

---


---

## 2-Input OR Gate

Truth Table

Input		Output
A	B	Y
0	0	
0	1	
1	0	
1	1	

Boolean Equation:

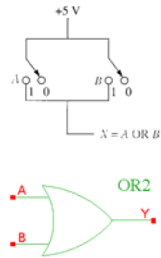


---

---

---

---

---

---

---

---

## Example – 2 Input OR Gate Timing Diagram

	t <sub>0</sub>	t <sub>1</sub>	t <sub>2</sub>	t <sub>3</sub>	t <sub>4</sub>	t <sub>5</sub>	t <sub>6</sub>	t <sub>7</sub>	t <sub>8</sub>	t <sub>9</sub>
A			1	1	0	0	1	1	0	0
B				1	1	1	0	0	1	1
Y										

---

---

---

---

---

---

---

---

### 3-Input OR

Input			Output
A	B	C	Y



Boolean Equation

---

---

---

---

---

---

---

---

---

---

### Example – 3 Input OR Gate Timing Diagram

	t <sub>0</sub>	t <sub>1</sub>	t <sub>2</sub>	t <sub>3</sub>	t <sub>4</sub>	t <sub>5</sub>	t <sub>6</sub>	t <sub>7</sub>	t <sub>8</sub>	t <sub>9</sub>
A	0	0	1	1	0	0	1	1	0	0
B	0	0	0	1	1	1	1	0	0	1
C	0	1	1	0	0	0	0	1	1	0
Y	0	1	1	1	1	1	1	0	1	0

---

---

---

---

---

---

---

---


---

---

### Example Circuit

Given the following Boolean equation,  
Wire it using the 74LS32 IC

$$X = A + B + C$$

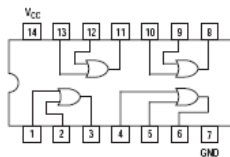


---

---

---

---

---

---


---

---

---

---

## Inverter (aka NOT Gate)

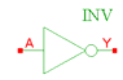

Boolean Equation:

Input		Output
A		Y

	t <sub>0</sub>	t <sub>1</sub>	t <sub>2</sub>	t <sub>3</sub>	t <sub>4</sub>	t <sub>5</sub>	t <sub>6</sub>	t <sub>7</sub>	t <sub>8</sub>	t <sub>9</sub>	t <sub>10</sub>
A											
Y											

---

---

---

---

---

---


---

---

## Example Circuit

Given the following Boolean equation,  
Wire it using the 74LS04 IC

$$Y = \overline{X}$$

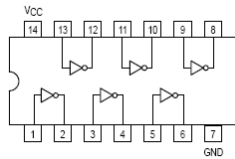


---

---

---

---


---

---

---

---

## 2 Input NAND Gate

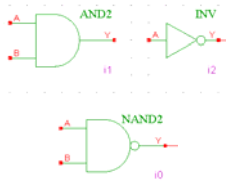

Boolean Equation

Input		Output
A	B	Y

---

---

---

---


---

---

---

---
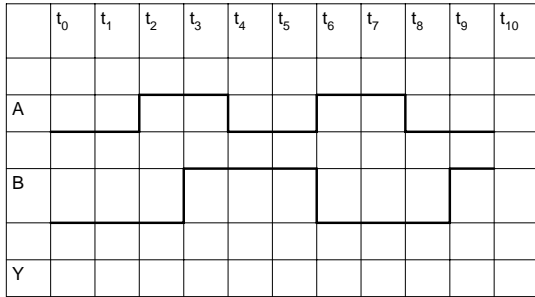
### Example – 2 Input NAND Gate Timing Diagram




---

---

---

---

---

---

---

---

---

---


---

---
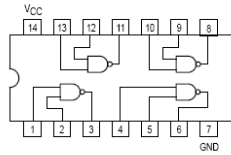
### Example Circuit

Given the following Boolean equation,  
Wire it using the 74LS00 IC

$$Z = \overline{\overline{X \bullet Y} \bullet D}$$




---

---

---

---

---

---

---

---


---

---

---

---

### 2 Input Nor Gate

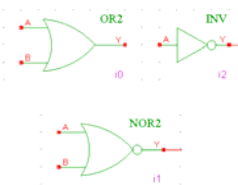

Input		Output
A	B	Y

Boolean Equation

---

---

---

---

---

---

---

---

---

---


---

---

## Example Circuit

Given the following Boolean equation,  
Wire it using the 74LS02 IC

$$N = \overline{H + I + J}$$

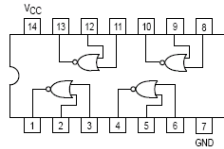

---

---

---

---

---

---

---

---

## Combinational Logic

Uses one or more basic logic gates to form a function. The inputs determine the output.

---

---

---

---

---

---

---

---

## Examples

Logic for automobile warning buzzer using combinational logic

- Buzzer activates if headlights are on and the driver's door is opened.
- Key is in the ignition and the driver's door is opened
- Motor is running, car in drive and the driver is NOT wearing a seatbelt.

---

---

---

---

---

---

---

---

## Example

Draw the circuit and fill in the truth table for the following boolean equation.

$$X = \bar{A} + B$$

	A	B	X

---

---

---

---

---

---

---


---

---

---
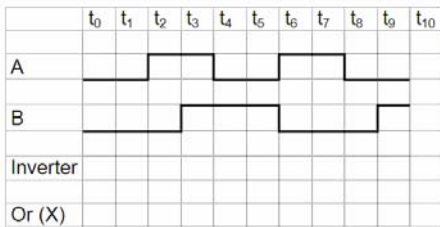
## Example Continued

- Complete the timing diagram for the last example




---

---

---

---

---

---

---


---

---

---
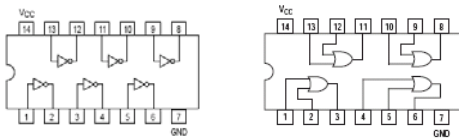
## Example Continued

- Connect the circuit from the previous example using a 74LS04 (inverter) and 74LS32 (OR) IC's.




---

---

---

---

---

---

---

---

---

---