

Lab #8  
I/O Card Part #2  
Output

**Purpose:**

To create an 8 bit output port.

**Procedure:**

Add the additional circuitry to your I/O card.

[This work can be done while waiting for the test equipment for Lab #7b to become available.]